


**AP[®] PHYSICS C - ELECTRICITY AND MAGNETISM
2014 SCORING GUIDELINES**

Question 1

15 points total

**Distribution
of points**

(a) 3 points

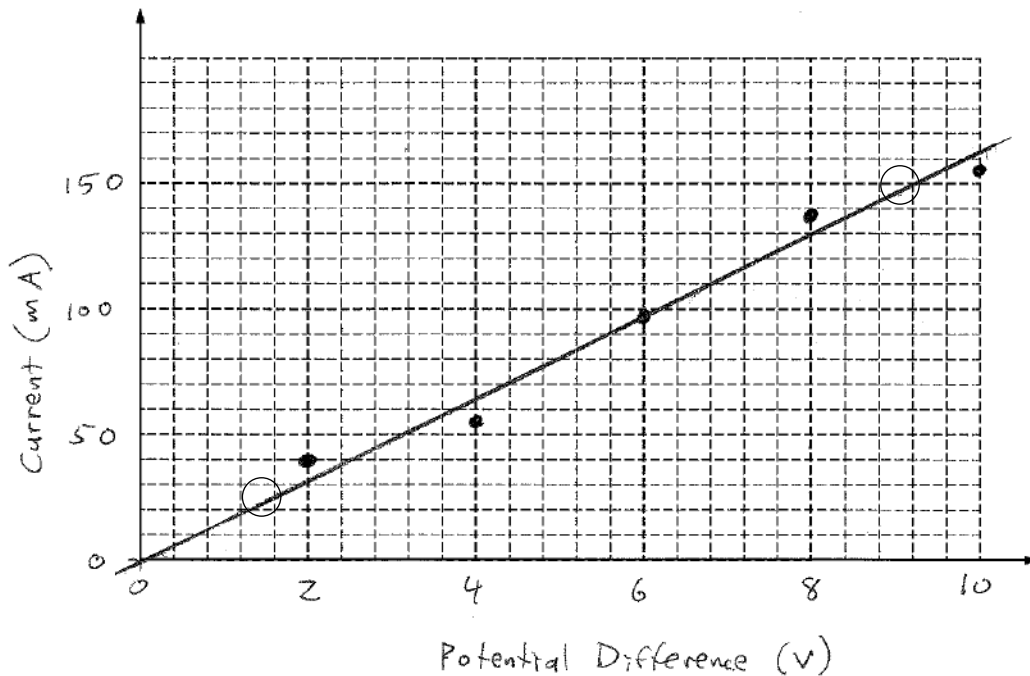

For labeling both axes with proper variables and units, and using appropriate linear scales for both axes

1 point

For properly plotting the data points

1 point

For drawing a reasonable best-fit straight line

1 point

(b) 3 points

For calculating a slope using points on the line drawn in part (a), not data points unless they are on that line

1 point

$$m = \frac{\Delta I}{\Delta V} = \frac{(150 - 25) \times 10^{-3} \text{ A}}{(9.2 - 1.6) \text{ V}} = 0.0164 \text{ A/V}$$

For correctly relating the slope to the resistance

1 point

$$V = IR$$

$$I = \frac{V}{R} = \frac{1}{R}V$$

$$\text{slope} = \frac{1}{R}$$

$$R = \frac{1}{\text{slope}} = \frac{1}{(0.0164 \text{ A/V})}$$

For an answer with correct units consistent with the calculated slope

1 point

$$R = 61 \Omega$$

Note: linear regression yields a slope of 0.01565 A/V and an answer of

$$R = 63.9 \Omega$$

**AP[®] PHYSICS C - ELECTRICITY AND MAGNETISM
2014 SCORING GUIDELINES**

Question 1 (continued)

		Distribution of points
(c)	2 points	
	For substituting the answer from part (b) into a correct equation to solve for R_1	1 point
	For recognizing that R_2 and R_3 are in series	1 point
	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2 + R_3}$ $\frac{1}{R_1} = \frac{1}{(R_T)} - \frac{1}{(R_2 + R_3)} = \frac{1}{(61 \Omega)} - \frac{1}{(50 \Omega + 50 \Omega)} = 0.0064/\Omega$ $R_1 = 156 \Omega$	
(d)	2 points	
	For using a correct equation to solve for I_2	1 point
	$I_2 = \frac{V}{R_2 + R_3}$ Substitute values $I_2 = \frac{(12 \text{ V})}{(50 \Omega + 50 \Omega)}$	
	For a correct answer with units	1 point
	$I_2 = 0.12 \text{ A}$	
(e) i.	1 point	
	For substituting proper values into a correct equation to solve for I_2	1 point
	$I_2 = \frac{V}{R_2} = \frac{(12 \text{ V})}{(50 \Omega)}$ $I_2 = 0.24 \text{ A}$	
ii.	2 points	
	For selecting "Less than"	1 point
	For a correct justification	1 point
	Example: After a long time, the capacitor is completely charged and there is no current in the capacitor branch because the voltage across the capacitor is equal to the battery voltage, so there is no current through or voltage drop across R_2 .	
	Note: If the wrong choice is selected, then no credit is given.	

**AP[®] PHYSICS C - ELECTRICITY AND MAGNETISM
2014 SCORING GUIDELINES**

Question 1 (continued)

		Distribution of points
(f)	2 points	
	For selecting “Equal to”	1 point
	For a correct justification	1 point
	Examples:	
	Immediately after the switch is closed, the uncharged capacitor has no resistance to current or it acts like a wire. Therefore it does not affect the current through R_2 .	
	The mathematical calculation in part (e)i does not depend on the value of C so changing the capacitance has no effect.	
	Note: If the wrong choice is selected, then no credit can be earned.	


PHYSICS C: ELECTRICITY AND MAGNETISM

SECTION II

Time—45 minutes

3 Questions

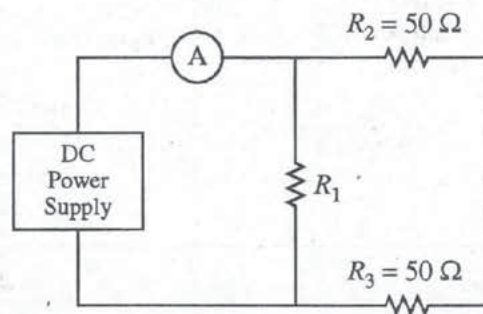Directions: Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in this booklet in the spaces provided after each part.




E&M. 1.

Physics students are analyzing the circuit above. A variable DC power supply is connected to an ammeter and three resistors. The resistances of two of the resistors are known to be $R_2 = R_3 = 50 \Omega$, but the resistance of the third resistor is unknown. The students collect data on the potential difference across the power supply and the current measured by the ammeter, as follows.

Potential Difference (V)	2	4	6	8	10
Current (mA)	40	55	97	138	155

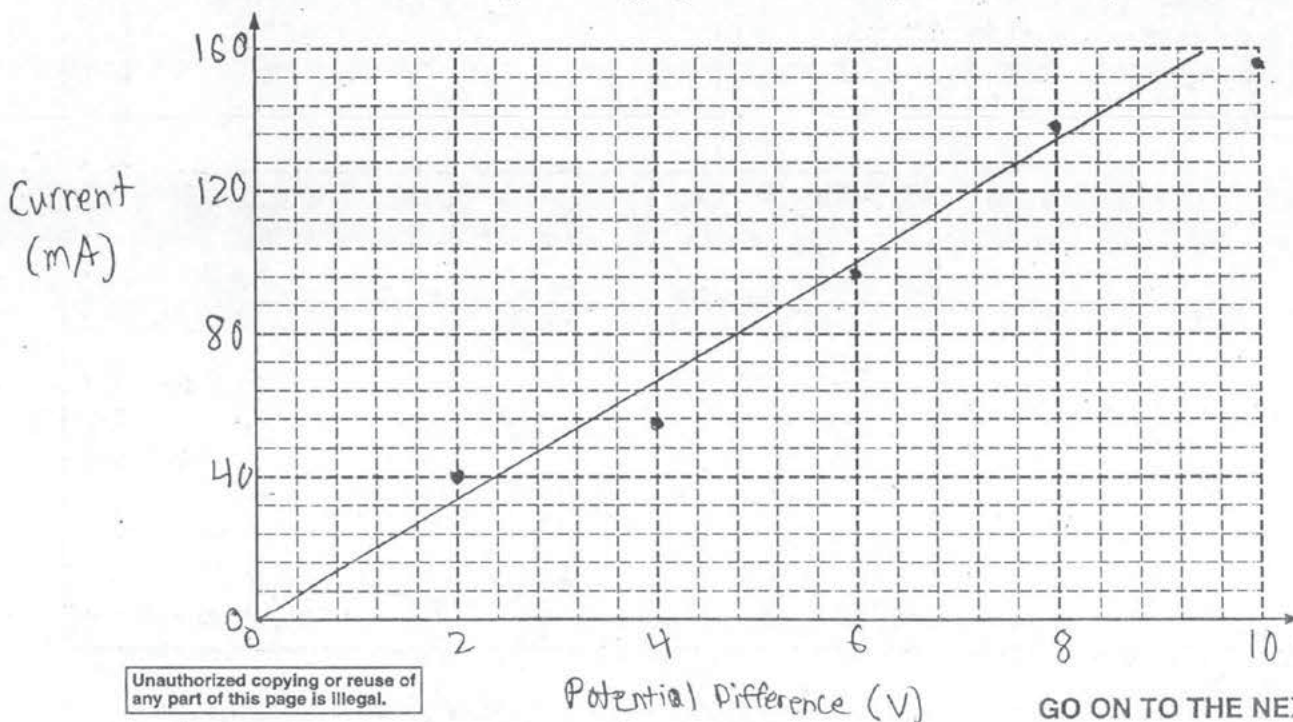- (a) On the grid below, plot the data points for the current as a function of the potential difference. Clearly scale and label all axes, including units if appropriate. Draw a straight line that best represents the data.



(b) Using the straight line from part (a), calculate the total resistance of the three-resistor combination.

$$R = \frac{V}{I} = \frac{6V}{100 \text{ mA}} = \frac{6V - 0V}{0.1A - 0.0A}$$

$$R_{\text{Tot}} = 60 \Omega$$

(c) Calculate the value of R_1 .



$$R' = R_2 + R_3 = 50 \Omega + 50 \Omega = 100 \Omega$$

$$R_1 = 150 \Omega$$

$$\frac{1}{R_{\text{Tot}}} = \frac{1}{R_1} + \frac{1}{R'}$$

$$\frac{1}{60} = \frac{1}{R_1} + \frac{1}{100} \quad \frac{1}{R_1} = \frac{1}{60} - \frac{1}{100} = \frac{5}{300} - \frac{3}{300} = \frac{2}{300} = \frac{1}{150}$$

The power supply is now fixed at 12 V.

(d) Calculate the current through R_2 .


$$R_{\text{Tot}} = 60 \Omega; V = 12V$$

$$I_{\text{net}} = \frac{V}{R_{\text{Tot}}} = \frac{1}{5} A$$

$$I_{R_2+R_3} = \frac{V}{R_2+R_3} = \frac{12V}{100 \Omega} = 0.12 A$$

$$I_{R_2} = 0.12 A$$

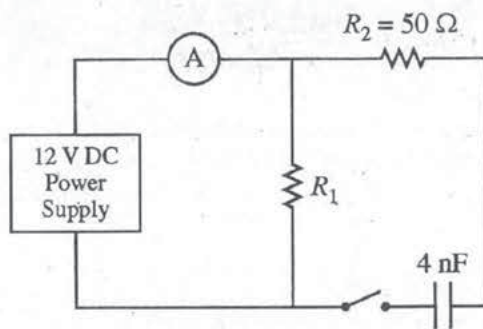- (e) Resistor 3 is now removed and replaced by an open switch in series with an uncharged 4 nF capacitor, as shown below. The power supply is still fixed at 12 V.



- i. Calculate the current in R_2 immediately after the switch is closed.

$$I_{R_2} = \frac{V}{R_2} = \frac{12\text{V}}{50\Omega} = 0.24\text{A}$$

- ii. A long time after the switch is closed, will the magnitude of the current in R_2 be greater than, less than, or equal to the current through R_2 found in part (d) ?

Greater than Less than Equal to

Justify your answer.

Once the voltage difference across the capacitor equals the voltage of the power supply, the capacitor will act as an open switch (not let any current through). Therefore, R_2 will have 0A of current flowing through it as well since it is in series with the capacitor.

- (f) The 4 nF capacitor is replaced with an uncharged 10 nF capacitor. Will the magnitude of the current in R_2 immediately after the switch is closed be greater than, less than, or equal to the current in part (e)i?

Greater than Less than Equal to

Justify your answer.

Before the capacitor starts storing charge, it has no voltage drop across it, and therefore acts like a piece of wire. Different capacitances have no effect in the instant after the switch is closed.


PHYSICS C: ELECTRICITY AND MAGNETISM

SECTION II

Time—45 minutes

3 Questions

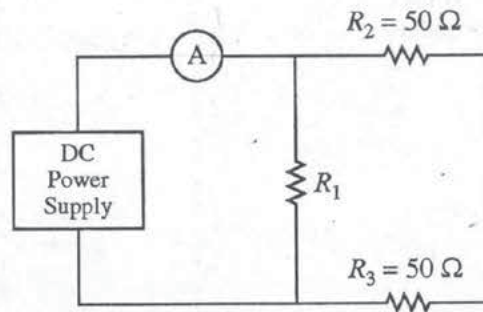Directions: Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in this booklet in the spaces provided after each part.




E&M. 1.

Physics students are analyzing the circuit above. A variable DC power supply is connected to an ammeter and three resistors. The resistances of two of the resistors are known to be $R_2 = R_3 = 50 \, \Omega$, but the resistance of the third resistor is unknown. The students collect data on the potential difference across the power supply and the current measured by the ammeter, as follows.

Potential Difference (V)	2	4	6	8	10
Current (mA)	40	55	97	138	155

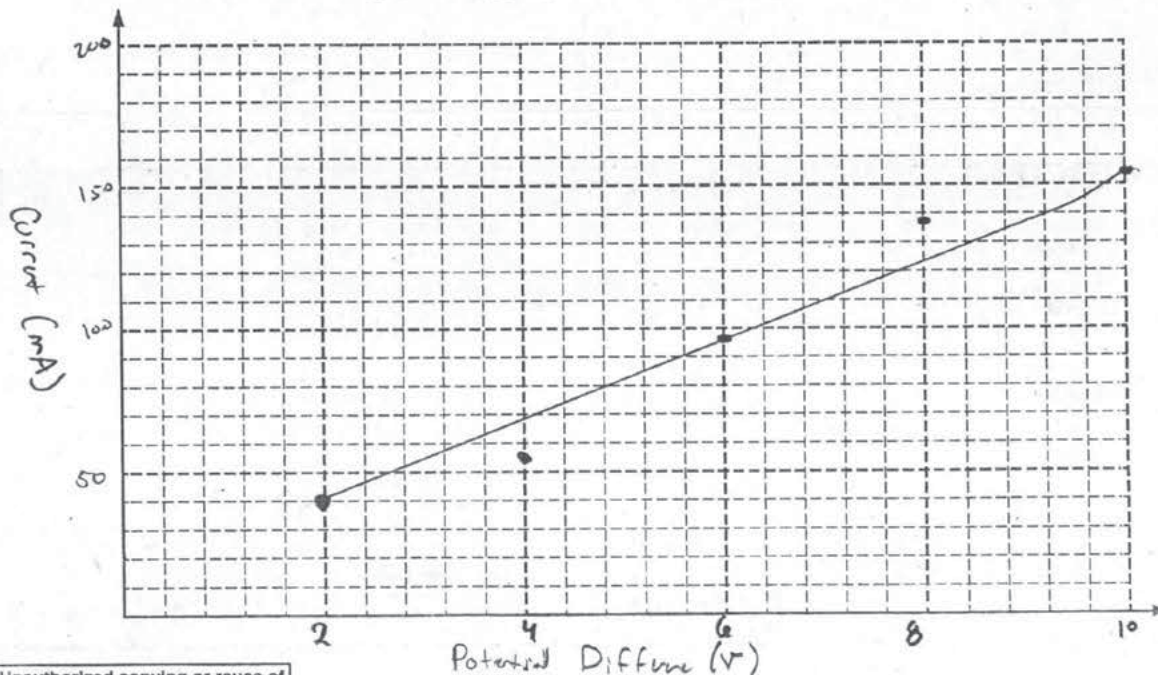- (a) On the grid below, plot the data points for the current as a function of the potential difference. Clearly scale and label all axes, including units if appropriate. Draw a straight line that best represents the data.



Unauthorized copying or reuse of
any part of this page is illegal.

GO ON TO THE NEXT PAGE.

(b) Using the straight line from part (a), calculate the total resistance of the three-resistor combination.

$$\Sigma R = \frac{\Sigma V}{\Sigma I}$$

$$\frac{1}{\Sigma R} = \frac{\Sigma I}{\Sigma V} = \frac{.155 - 0.04}{10 - 2} = .014735 = \frac{1}{\Sigma R}$$

$$\Sigma = 65.565 \Omega$$

(c) Calculate the value of R_1 .

$$R_2 + R_3 = R_{2+3}$$

$$50 + 50 = R_{2+3}$$

$$100 = R_{2+3}$$

$$\frac{1}{R_{2+3}} + \frac{1}{R_1} = \frac{1}{\Sigma R}$$

$$\frac{1}{100} + \frac{1}{R_1} = \frac{1}{65.565}$$

$$R_1 = 228.57 \Omega$$

The power supply is now fixed at 12 V.


(d) Calculate the current through R_2 .

$$E = 12 \text{ V} \quad V = IR$$

$$R_2 = 50 \Omega \quad 12 = I \cdot 50$$

$$0.24 \text{ A} = I$$

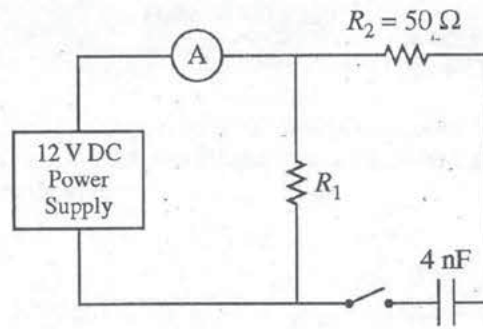- (e) Resistor 3 is now removed and replaced by an open switch in series with an uncharged 4 nF capacitor, as shown below. The power supply is still fixed at 12 V.



- i. Calculate the current in R_2 immediately after the switch is closed.

$$\begin{aligned}
 V &= IR & V &= IR & I_0 &= \frac{V}{R} \\
 12 &= I \cdot 50 & 12 &= I \cdot 50 & & \\
 0.24\text{A} &= I & 0.24\text{A} &= I & &
 \end{aligned}$$

- ii. A long time after the switch is closed, will the magnitude of the current in R_2 be greater than, less than, or equal to the current through R_2 found in part (d) ?

Greater than Less than Equal to

Justify your answer.

After a long period of time the capacitor is treated as if it were a simple wire due to the charge and capacitor reaching a level of equilibrium.

- (f) The 4 nF capacitor is replaced with an uncharged 10 nF capacitor. Will the magnitude of the current in R_2 immediately after the switch is closed be greater than, less than, or equal to the current in part (e)i?

Greater than Less than Equal to

Justify your answer.

The increase in capacitance will affect the amount of both charge and current to reach the resistor, lowering the both as the capacitor begins to charge.


PHYSICS C: ELECTRICITY AND MAGNETISM

SECTION II

Time—45 minutes

3 Questions

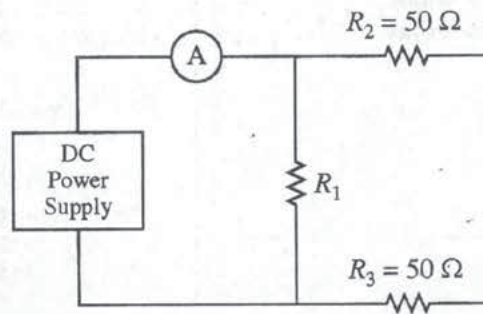Directions: Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in this booklet in the spaces provided after each part.




E&M. 1.

Physics students are analyzing the circuit above. A variable DC power supply is connected to an ammeter and three resistors. The resistances of two of the resistors are known to be $R_2 = R_3 = 50 \Omega$, but the resistance of the third resistor is unknown. The students collect data on the potential difference across the power supply and the current measured by the ammeter, as follows.

Potential Difference (V)	2	4	6	8	10
Current (mA)	40	55	97	138	155

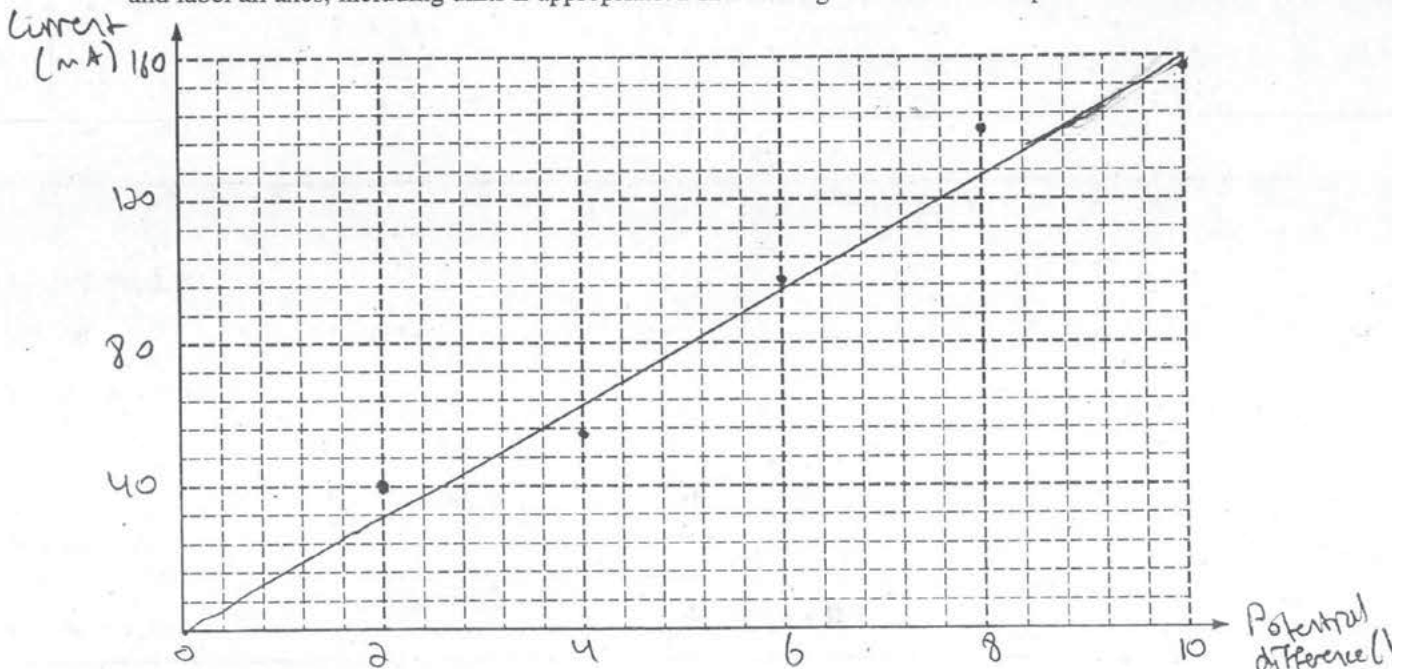- (a) On the grid below, plot the data points for the current as a function of the potential difference. Clearly scale and label all axes, including units if appropriate. Draw a straight line that best represents the data.




Unauthorized copying or reuse of
any part of this page is illegal.

GO ON TO THE NEXT PAGE.

(b) Using the straight line from part (a), calculate the total resistance of the three-resistor combination.

$$\begin{aligned} & (2.6, 120) \\ & (2.6, 56) \\ & \frac{120 - 56}{2.6 - 2.6} = \frac{64}{4} = 16 = .016 \text{ amps/volt} \\ & \qquad \qquad \qquad 62.5 \text{ volts/amp} \\ & \frac{V}{I} = R \quad R = 62.5 \end{aligned}$$

(c) Calculate the value of R_1 .
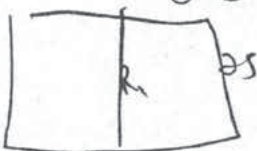
$$\left(\frac{1}{50} + \frac{1}{80}\right)^{-1} = 25$$


$$62.5 = 25 + R_1$$


$$R_1 = 37.5 \Omega$$

The power supply is now fixed at 12 V.

(d) Calculate the current through R_2 .

$$V = IR$$


$$12 = I \cdot 80$$
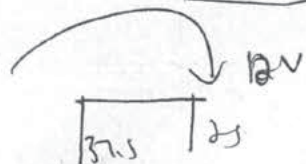
$$I = .24$$

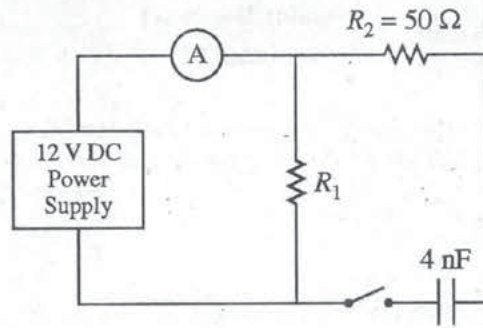
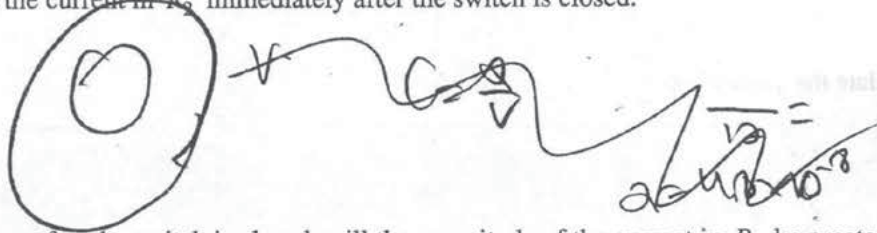
$$12 = I \cdot 80$$

$$I = \frac{1}{2}$$

- (e) Resistor 3 is now removed and replaced by an open switch in series with an uncharged 4 nF capacitor, as shown below. The power supply is still fixed at 12 V .



- i. Calculate the current in R_2 immediately after the switch is closed.



- ii. A long time after the switch is closed, will the magnitude of the current in R_2 be greater than, less than, or equal to the current through R_2 found in part (d) ?

Greater than Less than Equal to

Justify your answer.

The capacitor will be fully charged after awhile so the voltage will be going through as if it was not there as in part (d).

- (f) The 4 nF capacitor is replaced with an uncharged 10 nF capacitor. Will the magnitude of the current in R_2 immediately after the switch is closed be greater than, less than, or equal to the current in part (e)i?

Greater than Less than Equal to

Justify your answer.

The capacitor is greater and uncharged, so the current will be hindered because the capacitor has to charge and even after it charges it will still allow less current to go through at a time.

AP[®] PHYSICS C: ELECTRICITY AND MAGNETISM

2014 SCORING COMMENTARY

Question 1

Overview

This question involved an experiment where voltage was varied and current was measured. In addition to assessing data analysis, the question was intended to assess student understanding of RC circuits, especially the loop rule. It required students to use data to make a graph of current versus voltage to determine resistance, to solve a few simple loop rule questions, and then to answer and justify questions about capacitor charging behavior.

Sample: E1 A

Score: 15

This response earned full credit in all parts. It also has clear justifications in parts (e)(ii) and (f) that identify the physical reasons why a capacitor acts like an open or a short circuit.

Sample: E1 B

Score: 9

This response earned full credit in parts (a) and (b). Since the best fit line was drawn through two original data points, those points are acceptable to use to calculate the slope. Part (c) also earned full credit, even though the final answer was incorrect, since the points were awarded for understanding the correct procedure and not the final answer. Part (d) earned no credit. Part (e)(i) earned full credit, but parts (e)(ii) and (f) earned zero points because the selections were incorrect.

Sample: E1 C

Score: 5

This response earned full credit in part (a). Part (b) lost 1 point because the final answer has no units. In part (c) the calculation treats R_2 and R_3 as if they were in parallel and then treats their sum as if it was in series with R_1 , so no points were earned. In part (d) the response does not include both R_2 and R_3 , and no points were earned. No credit was earned for parts (e) or (f).